

Flip-Flops

Digital Logic Design (CC131)
BSCS 2nd Semester Spring-2026

By

Syed Zulfiqar Ali Shah,

Associate Professor (CS) / HoD

Govt. College of Management Sciences, Kohat

www.linkedin.com/in/syedzulfiqaralishah

Flip-Flops

- A Flip-flop is a fundamental building block of Sequential Logic circuits.
- It is a Synchronous bistable multivibrator which means it has two stable states (represented as 0 and 1).
- Synchronous means it acts with respect to another object, called Clock.
- It can store One bit of digital data.
- The output of a flip-flop depends on both its current inputs and its previous state.

Flip-Flops



- The Clock (CLK) input is the most important control signal which distinguishes it from a Latch.
- The clock has a special component called Edge-Detector, which makes sure that the Flip-flop only looks at the data input at the specific transition of the pulse (rising edge or falling edge).
- Flip-flops are edge-triggered or edge-sensitive devices.

Flip-Flops


- The edge-triggered flip-flop changes its state only at the positive edge (rising edge) or at the negative edge (falling edge) of the clock pulse.
- It looks on the input only when the specified (positive edge or negative edge) clock transition occurs and flips its state accordingly.
- A small triangle at the Clock input (C), in its symbol, is called Dynamic input indicator and this is the identification mark of an edge-triggered flip-flop.

SYMBOLS


Positive Edge-Triggered Flip-Flops

 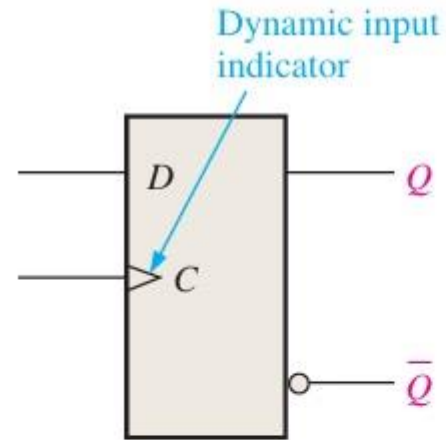

Negative Edge-Triggered Flip-Flops

 

(a) D

 

(b) J-K

APPLICATIONS of Flip-Flops

Data Storage: basic unit of memory in registers and Cache

Counters: counts pulses or events in digital systems

State Machines: stores “current state” in complex controllers and processors

TYPES of Flip-Flops

Two types are discussed.

1. D Flip-flop
2. J-K Flip-flop


D Flip-Flops

- The Data flip-flop has an input D which is reflected on the output Q only on the triggering edge of the clock pulse.
- D is called synchronous input.
- **SET State:**


When D is HIGH, the Q also goes HIGH on the triggering edge of the clock pulse.
- **RESET State:**

When D is LOW, the Q also goes LOW on the triggering edge of the clock pulse.

 Operation of a Positive edge-triggered D Flip-Flop.



 (a) $D = 1$ flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



(b) $D = 0$ flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)

REMEMBER:

- Q follows D at the triggering edge of the clock pulse.
- The flip-flop cannot change its state except on the triggering edge of the clock pulse.

Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
D	CLK	Q	$\overline{Q}$	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH

Example

Determine the Q and $\overline{Q}$ output waveforms of the flip-flop in Figure 7–15 for the D and CLK inputs in Figure 7–16(a). Assume that the positive edge-triggered flip-flop is initially RESET.

 


FIGURE 7-15

 


FIGURE 7-16

EXAMPLE 7-4

Determine the Q and $\overline{Q}$ output waveforms of the flip-flop in Figure 7-15 for the D and CLK inputs in Figure 7-16(a). Assume that the positive edge-triggered flip-flop is initially RESET.

 


FIGURE 7-15

 


FIGURE 7-16

Solution

1. At clock pulse 1, D is LOW, so Q remains LOW (RESET).
2. At clock pulse 2, D is LOW, so Q remains LOW (RESET).
3. At clock pulse 3, D is HIGH, so Q goes HIGH (SET).
4. At clock pulse 4, D is LOW, so Q goes LOW (RESET).
5. At clock pulse 5, D is HIGH, so Q goes HIGH (SET).
6. At clock pulse 6, D is HIGH, so Q remains HIGH (SET).

Once Q is determined, $\overline{Q}$ is easily found since it is simply the complement of Q .

J-K Flip-Flops

➤ The J-K flip-flop has two synchronous inputs J and K.

➤ **SET State:**

When J is HIGH and K is LOW,
the Q goes HIGH on the triggering edge of the clock pulse.

➤ **RESET State:**

When J is LOW and K is HIGH,
the Q goes LOW on the triggering edge of the clock pulse





➤ **No Change State:**

When both J and K are LOW,
the Output does not change from its previous state.

➤ **TOGGLE Mode:**

When both J and K are HIGH,
the flip-flop changes state.

    Operation of a Positive edge-triggered J-K Flip-Flop.



Truth table for a positive edge-triggered J-K flip-flop.

Inputs			Outputs		Comments
J	K	CLK	Q	$\overline{Q}$	
0	0	↑	Q_0	$\overline{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\overline{Q}_0$	Q_0	Toggle

↑ = clock transition LOW to HIGH

Q_0 = output level prior to clock transition

Example

The waveforms in Figure 7–18(a) are applied to the J , K , and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially RESET.


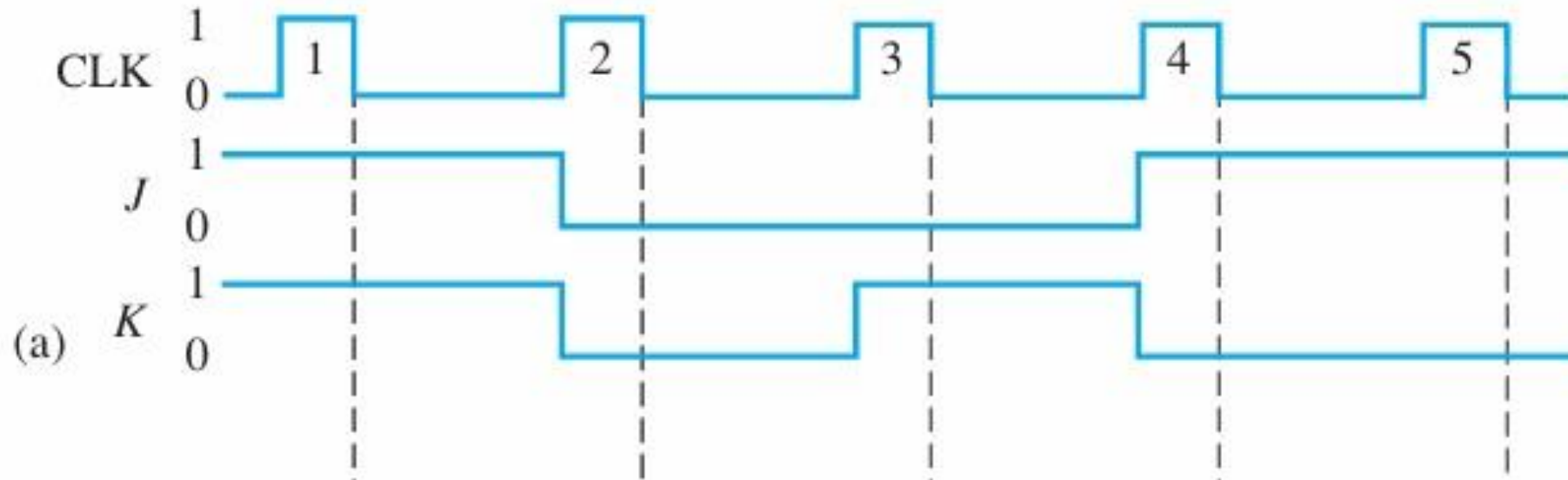


FIGURE 7–18

 

EXAMPLE 7-5

The waveforms in Figure 7-18(a) are applied to the J , K , and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially RESET.

 
 


FIGURE 7-18

EXAMPLE 7-5

The waveforms in Figure 7-18(a) are applied to the J , K , and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially RESET.

 


FIGURE 7-18

Solution

Since this is a negative edge-triggered flip-flop, as indicated by the “bubble” at the clock input, the Q output will change only on the negative-going edge of the clock pulse.

1. At the first clock pulse, both J and K are HIGH; and because this is a toggle condition, Q goes HIGH.
2. At clock pulse 2, a no-change condition exists on the inputs, keeping Q at a HIGH level.
3. When clock pulse 3 occurs, J is LOW and K is HIGH, resulting in a RESET condition; Q goes LOW.
4. At clock pulse 4, J is HIGH and K is LOW, resulting in a SET condition; Q goes HIGH.
5. A SET condition still exists on J and K when clock pulse 5 occurs, so Q will remain HIGH.

Thank You