

Up / Down Synchronous Counters

Digital Logic Design (CC131)

BSCS 2nd Semester Spring-2026

By

Syed Zulfiqar Ali Shah,

Associate Professor (CS) / HoD

Govt. College of Management Sciences, Kohat

www.linkedin.com/in/syedzulfiqaralishah

UP/DOWN COUNTER

- An **up/down counter** is a digital circuit that can **count upwards** ($0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \dots$) or **downwards** ($7 \rightarrow 6 \rightarrow 5 \rightarrow 4 \dots$) depending on a control signal.
- **UP mode**: Counts forward.
- **DOWN mode**: Counts backward.
- One pin (called **UP/DOWN**) decides the direction:
 - **HIGH** = Up counting
 - **LOW** = Down counting

Example : 3-Bit Binary Up/Down Counter

A 3-bit counter has 3 flip-flops: Q_2 Q_1 Q_0 (Q_0 is the Least Significant Bit).


UP Sequence:

0 (000) $\rightarrow$ 1 (001) $\rightarrow$ 2 (010) $\rightarrow$ 3 (011) $\rightarrow$ 4 (100) $\rightarrow$ 5 (101) $\rightarrow$ 6 (110) $\rightarrow$ 7 (111) $\rightarrow$ 0...

DOWN Sequence:

0 (000) $\leftarrow$ 1 (001) $\leftarrow$ 2 (010) $\leftarrow$ 3 (011) $\leftarrow$ 4 (100) $\leftarrow$ 5 (101) $\leftarrow$ 6 (110) $\leftarrow$ 7 (111)

Example : 3-Bit Binary Up/Down Counter

 

How Do We Make It Count? (The Logic)

The core idea: J-K Flip-Flops

- Each bit of the counter is stored in a J-K flip-flop (FF0, FF1, FF2).
- A flip-flop *toggles* (changes state) when its J and K inputs are both 1.
- So the trick is: *make $J=K=1$ only at the right moment.*

Example : 3-Bit Binary Up/Down Counter

1. FF0 (LSB - Q_0)

- Always toggles on every clock pulse (both in UP and DOWN mode).

So: $J_0 = K_0 = 1$ (always)

This is same for both directions.

2. FF1 (Q_1) When should Q_1 toggle?

- In **UP mode**: Q_1 toggles when $Q_0 = 1$
- In **DOWN mode**: Q_1 toggles when $Q_0 = 0$

We combine both using the UP/DOWN control signal:

$$J_1 = K_1 = (Q_0 \cdot \text{UP}) + (\overline{Q_0} \cdot \text{DOWN})$$

Simple meaning:

- If UP is active $\rightarrow$ use Q_0
- If DOWN is active $\rightarrow$ use $\overline{Q_0}$

3. FF2 (Q₂) - Most Significant Bit

When should Q₂ toggle?

- In **UP mode**: Both lower bits must be 1 $\rightarrow Q_1 \cdot Q_0 = 1$
- In **DOWN mode**: Both lower bits must be 0 $\rightarrow \overline{Q_1} \cdot \overline{Q_0} = 1$

So the equation becomes:

$$J_2 = K_2 = (Q_1 \cdot Q_0 \cdot \text{UP}) + (\overline{Q_1} \cdot \overline{Q_0} \cdot \text{DOWN})$$


The equations are built from one simple pattern —
"a flip-flop toggles only when all the lower bits are at their boundary value".

For counting UP that boundary is all-1s.
For counting DOWN it's all-0s.

The UP/DOWN control signal just selects which condition applies, using basic AND and OR logic gates.


EXAMPLE 9-3

Show the timing diagram and determine the sequence of a 4-bit synchronous binary up/down counter if the clock and $UP/\overline{DOWN}$ control inputs have waveforms as shown in Figure 9-23(a). The counter starts in the all-0s state and is positive edge-triggered.

 

EXAMPLE 9-3

Show the timing diagram and determine the sequence of a 4-bit synchronous binary up/down counter if the clock and $UP/\overline{DOWN}$ control inputs have waveforms as shown in Figure 9-23(a). The counter starts in the all-0s state and is positive edge-triggered.

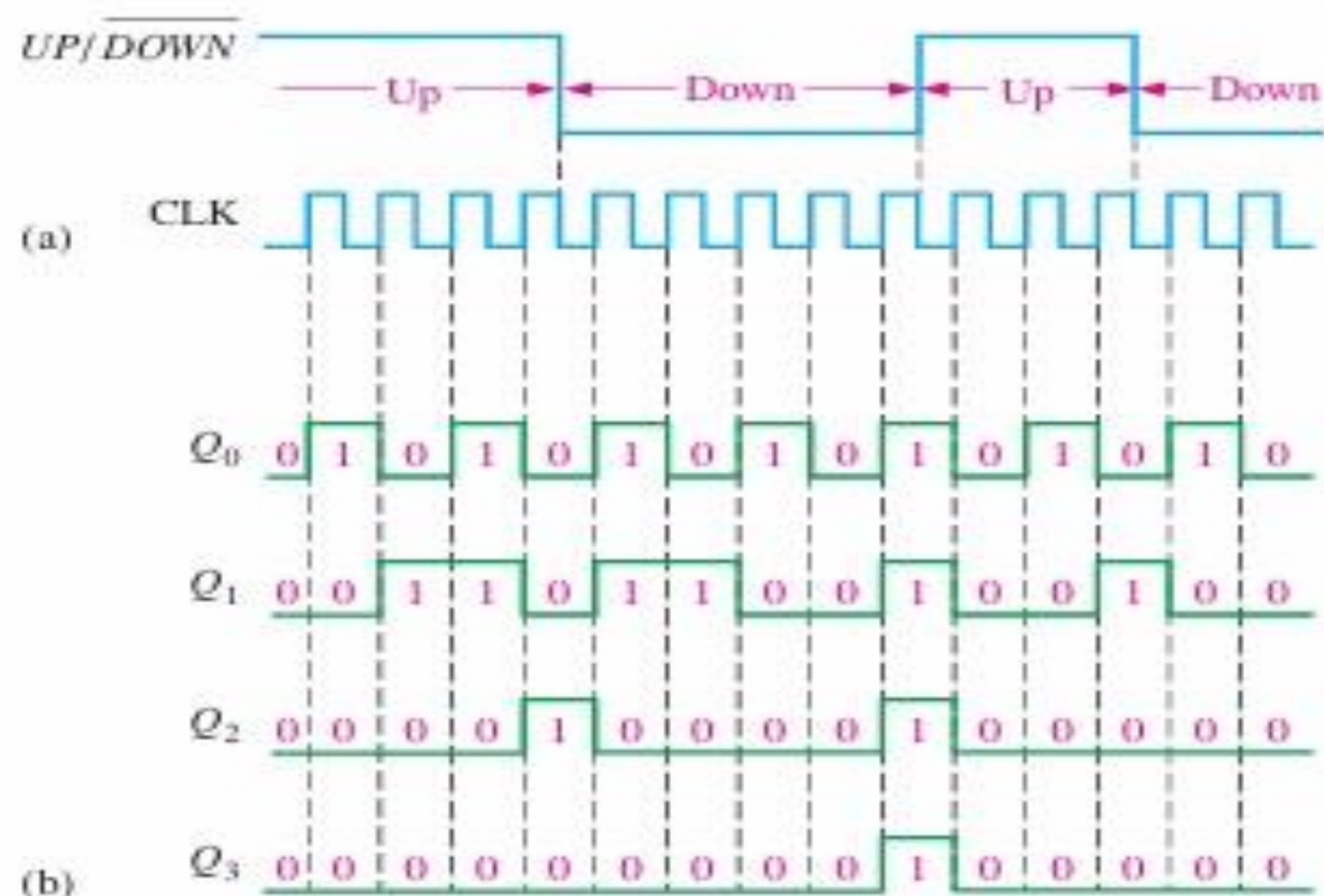**FIGURE 9-23**

Thank You